OSCILLATION IN AN A- β BOX

If a system contains a frequency of phase reversal (has 3 or more frequency corners) then oscillation may occur when there is a loop gain of at least 1, i.e. $\beta |A(j\omega)| = 1$ at the frequency of phase reversal.

The Problem:



Find the frequency of phase reversal f_{θ}

Use the expression:

$$-180 = -\tan^{-1}\frac{f_0}{10^4} - 2\tan^{-1}\frac{f_0}{10^5}$$

By trial and error, it can be determined that $f_0 = 1.096 \times 10^5$ Hz. This is the frequency of phase reversal.

Find the minimum value of β for which oscillation will occur

First, evaluate $A(j\omega)$ at the frequency of phase reversal f_0 , and find the magnitude of the A-box gain. $A(j\omega) = \frac{1000}{\left(1 + j\frac{1.096 \times 10^5}{10^4}\right)\left(1 + j\frac{1.096 \times 10^5}{10^5}\right)^2}$ $|A(j\omega)| = 41.28$

Now we find the value of β for which the magnitude of the loop gain is one.

$$1 = \beta |A(f_1)| = 41.28\beta$$
$$\beta = 0.02422$$

What value of β would result in a gain margin of 10 dB?

In other words, what value of β would result in the loop gain being 10 dB **below** 0 dB at the frequency of phase reversal?

First, convert the value of **negative** 10 $10^{(-10/20)} = 0.3162 \text{ V/V}$ dB to units of V/V.

Then find the value of b that would result in this gain.

 $\beta |A(j\omega)| = 0.3162$ $\beta = \frac{0.3162}{0.4128}$ $\beta = 0.7660$

Find the gain margin when β is given

If β is known to be 0.001, what is the gain margin? In other words, by how many dB is the loop gain **below** 0 dB at the frequency of phase reversal?

First, find the loop gain magnitude at phase reversal. Convert to decibels and change the sign to positive. $\beta |A(j\omega)| = 0.04128$ $20 \log 0.04128 = -27.69 \text{ dB}$ Gain Margin = 27.69 dB

What value of β would result in a phase margin of 45°?

Use the expression:

$$-180 + 45 = -\tan^{-1}\frac{f_1}{10^4} - 2\tan^{-1}\frac{f_1}{10^5}$$

By trial and error, it can be determined that $f_1 = 5.285 \times 10^4$ Hz. This is the frequency at which the amplifier is 45° from phase reversal.

