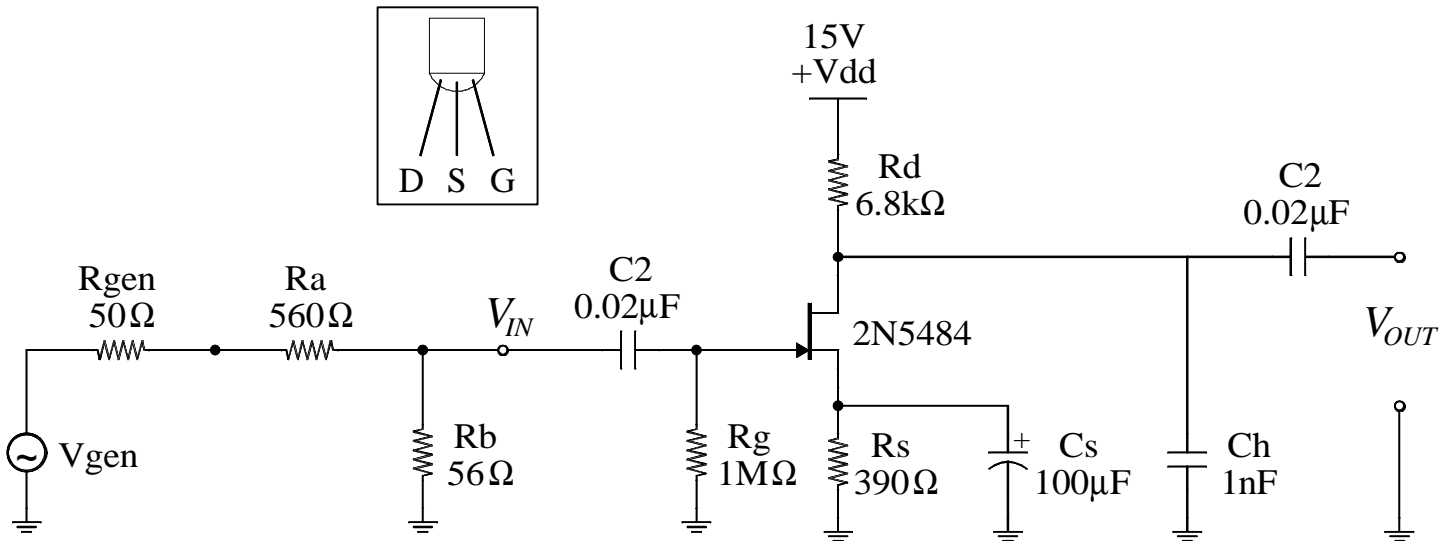


FET EXPERIMENT

Lab 1 Notes – EE 321K



Given for the prep:

Drain current when in saturation: $I_{DSS} = 2.5 \text{ mA}$

Pinch-off voltage: $V_p = -1 \text{ V}$

Gate current: $I_G = 0 \text{ mA}$

Slope of output characteristic in saturation $Y_{OS} = 0 \text{ } \Omega^{-1}$

TRANSFER CHARACTERISTIC

The relationship between the drain current and the gate-to-source voltage with the FET in saturation.

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2$$

DC LOAD LINE

The relationship between the drain current and the gate-to-source voltage with the gate at ground potential.

$$I_D = -\frac{1}{R_s} V_{GS}$$

V_{GSQ} , I_{DQ} Q POINT

The DC operating point of the FET, found at the intersection of the above two functions; the point at (V_{GSQ}, I_{DQ}) .

SATURATION REGION

The FET is in the saturation region when $V_{DS} > |V_p|$.


V_{GSQ} DRAIN-TO-SOURCE OPERATING VOLTAGE

The drain-to-source voltage present when the FET is operating at the Q-point.

$$V_{DSQ} = V_{DQ} - V_{SQ} = (V_{DD} - I_{DQ} R_d) - I_{DQ} R_s$$

Y_{fs} TRANSCONDUCTANCE

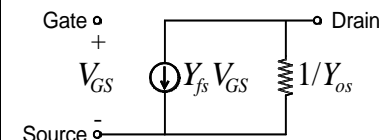The transconductance of the FET model is the rate of change of the drain current in response to a change in the gate-to-source voltage, or the slope of the transfer characteristic curve at the Q-point.




$$Y_{fsQ} = g_m = \left| \frac{\partial I_D}{\partial V_{GS}} \right|$$

Y_{os} OUTPUT TRANSCONDUCTANCE

The output transconductance of the FET model is the rate of change of the drain current as a function the drain-to-source voltage, or the slope of the output characteristic at the Q-point.


$$Y_{os} = \frac{1}{r_o} = \left| \frac{\partial I_D}{\partial V_{DS}} \right|$$

PSPICE MODEL Lab1withCs.sch

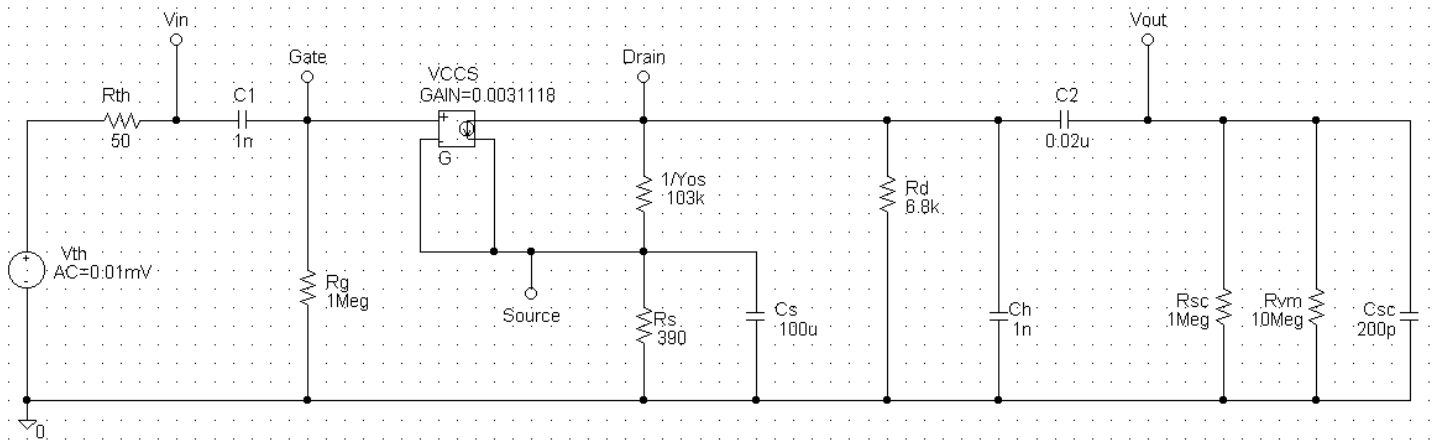

FREQUENCY CORNERS DUE TO C_S

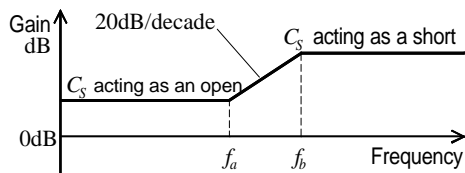The capacitor C_S produces two frequency corners f_a and f_b with a 20dB/decade slope in between.



At f_a , the reactance of C_S is equal to R_S .
$$f_a = \frac{1}{2\pi C_S R_S}$$

$$f_b = f_a (1 + Y_{fs} R_S) = \frac{1}{2\pi C_S [R_S \parallel (1/Y_{fs})]}$$

by "looking" into the circuit from C_S

DISTORTION ANALYSIS

Given an input sinewave of 0.12V peak.

$$V_{GS} = V_{GSQ} + 0.12 \sin \omega t$$

What is the percent second harmonic distortion?
Using the transfer function:

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

Only this term needs to be evaluated.

Evaluate:

$$\left(1 - \frac{V_{GSQ} + 0.12 \sin \omega t}{V_P} \right)^2 = \left(1 - \frac{-0.38 + 0.12 \sin \omega t}{-1} \right)^2$$

$$= (0.62 + 0.12 \sin \omega t)^2 = (0.0144 \sin^2 \omega t + 0.148 \sin \omega t + 0.3844)$$

Taking the coefficients from the first and second

harmonic: % 2nd harmonic = $\frac{0.0144}{0.1488} \times 100 = 9.6774\%$

FREQUENCY CORNER DUE TO C_1

The capacitor C_1 produces a low frequency corner.

$$f_{L1} = \frac{1}{2\pi C_1 (R_{th} + R_g)}$$

FREQUENCY CORNER DUE TO C_2

The capacitor C_2 produces a low frequency corner.

$$f_{L2} = \frac{1}{2\pi C_2 [R_d + (R_{VM} \parallel R_{SC})]}$$

FREQUENCY CORNER DUE TO C_h and C_{sc}

The capacitor C_h and the capacitance due to cables and instruments C_{sc} produce a high frequency corner.

$$f_H = \frac{1}{2\pi (C_h + C_{sc}) (R_d \parallel R_{VM} \parallel R_{SC})}$$

